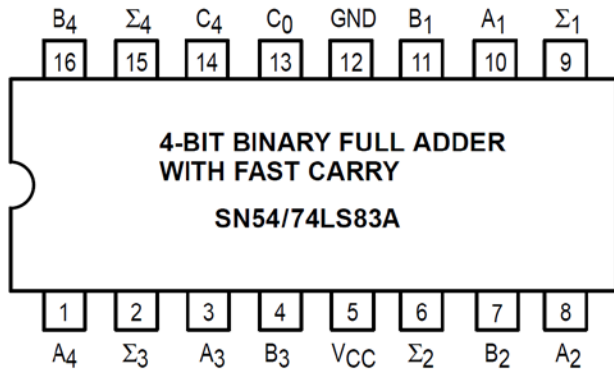


Experiment 4

In this, we shall study and use IC 7483 which performs 4-bit addition / subtraction.



PIN NAMES

A ₁ –A ₄	Operand A Inputs
B ₁ –B ₄	Operand B Inputs
C ₀	Carry Input
Σ ₁ –Σ ₄	Sum Outputs (Note b)
C ₄	Carry Output (Note b)

NOTES:


a) 1 TTL Unit Load (U.L.) = 40 μA HIGH/1.6 mA LOW.

b) The Output LOW drive factor is 2.5 U.L. for Military (54) and 5 U.L. for Commercial (74) Temperature Ranges.


LOADING (Note a)

HIGH	LOW
1.0 U.L.	0.5 U.L.
1.0 U.L.	0.5 U.L.
0.5 U.L.	0.25 U.L.
10 U.L.	5 (2.5) U.L.
10 U.L.	5 (2.5) U.L.

LOGIC DIAGRAM

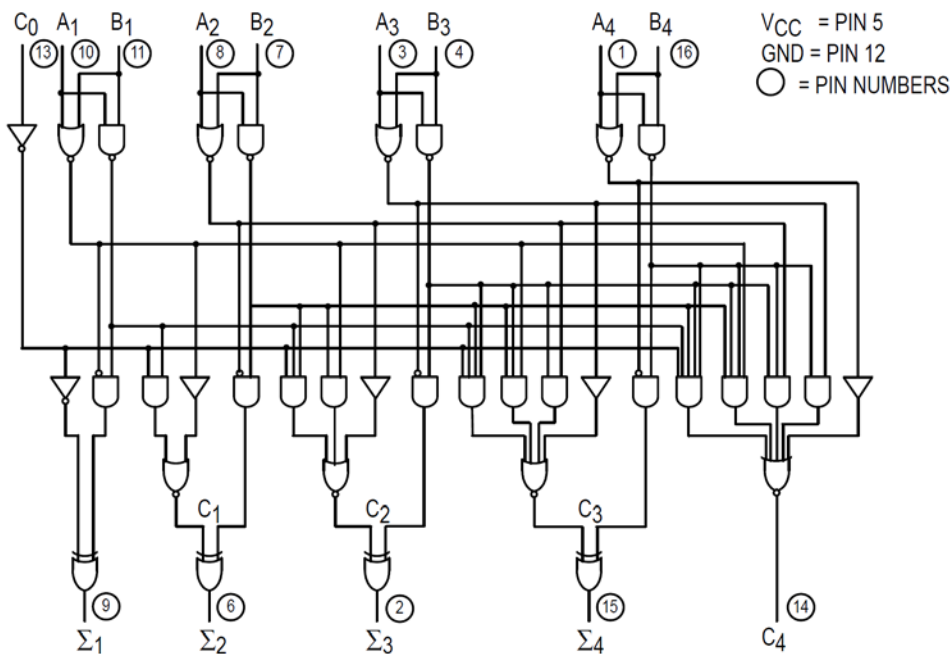

LOGIC SYMBOL

 

DC CHARACTERISTICS OVER OPERATING TEMPERATURE RANGE (unless otherwise specified)

Symbol	Parameter	Limits			Unit	Test Conditions
		Min	Typ	Max		
V _{IH}	Input HIGH Voltage	2.0			V	Guaranteed Input HIGH Voltage for All Inputs
V _{IL}	Input LOW Voltage	54		0.7	V	Guaranteed Input LOW Voltage for All Inputs
		74		0.8		
V _{IK}	Input Clamp Diode Voltage		–0.65	–1.5	V	V _{CC} = MIN, I _{IN} = –18 mA
V _{OH}	Output HIGH Voltage	54	2.5	3.5	V	V _{CC} = MIN, I _{OH} = MAX, V _{IN} = V _{IH} per Truth Table
		74	2.7	3.5	V	
V _{OL}	Output LOW Voltage	54, 74	0.25	0.4	V	V _{CC} = V _{CC} MIN, V _{IN} = V _{IL} or V _{IH} per Truth Table
		74	0.35	0.5	V	
I _{IH}	Input HIGH Current C ₀ A or B			20 40	μA	V _{CC} = MAX, V _{IN} = 2.7 V
	C ₀ A or B			0.1 0.2	mA	V _{CC} = MAX, V _{IN} = 7.0 V
I _{IL}	Input LOW Current C ₀ A or B			–0.4 –0.8	mA	V _{CC} = MAX, V _{IN} = 0.4 V

AC CHARACTERISTICS ($T_A = 25^\circ\text{C}$)

Symbol	Parameter	Limits			Unit	Test Conditions
		Min	Typ	Max		
t_{PLH} t_{PHL}	Propagation Delay, C_0 Input to any Σ Output		16 15	24 24	ns	$V_{CC} = 5.0\text{ V}$ $C_L = 15\text{ pF}$ Figures 1 and 2
t_{PLH} t_{PHL}	Propagation Delay, Any A or B Input to Σ Outputs		15 15	24 24	ns	
t_{PLH} t_{PHL}	Propagation Delay, C_0 Input to C_4 Output		11 15	17 22	ns	
t_{PLH} t_{PHL}	Propagation Delay, Any A or B Input to C_4 Output		11 12	17 17	ns	

AC WAVEFORMS

 


Figure 1

 


Figure 2

What would have been propagation delay for C_0 input to C_4 output had it not been fast adder?

Task 1: Design a circuit that can perform both 4-bit addition and subtraction in which an input Mode = 0 refers to addition and Mode = 1 refers to subtraction.

Additional: Consider, an additional sign bit is available at the output which if 0, the number is positive and if 1, the number is negative. Show, how a result of subtraction can be read in standard binary form (not 2's complement form in association with sign bit for negative result).

Use LED display of trainer kit to show result and also give input for 4-bit numbers from trainer kit.

Consider the 4 bit addition of Task 1 above where you want to show the result in 7 segment display. If the result is more than 9, say $5 + 7 = 12$, then a specific character corresponding to 1100 will appear and not digit 2 in unit's place.

It is interesting to note that whenever a number above 9 is to be displayed, adding 6 to that number will generate appropriate BCD for unit's place. Can you tell why so? For previous example of displaying 12: $1100 + 0110 = 1\ 0010$ or $(000)1\ 0010$ i.e. least significant 4 bits 0010 can be used for displaying 2 in unit's place and the carry (generated by another IC 7483 that can be used for addition of 0110) can be sent for displaying BCD of ten's place i.e. $0001 = 1$.

Take another example: $9 + 8 = 17$ which is 10001. For BCD display, add 6 i.e. $10001 + 0110 = 10111 = (000)1\ 0111$

Note that, 0110 is to be added only when the result of addition is more than 9 and not always.

Task 2: Use two IC 7483 and appropriate combinatorial logic circuit to display result of binary addition of two 4-bit numbers in BCD format through 7-segment display.

Additional: Show how subtraction result can be displayed in BCD format where decimal point of 7 segment can be considered as sign bit.