

Experiment on Implementing (4x4)-bit Serial-Parallel Multiplier

04/11/2020

$a_3 a_2 a_1 a_0$ - multiplicand
 $b_3 b_2 b_1 b_0$ - multiplier

| | | | | | | | | |
|-------------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| PP ₀ : | $a_3 b_0$ | $a_2 b_0$ | $a_1 b_0$ | $a_0 b_0$ | | | | |
| PP ₁ : | $a_3 b_1$ | $a_2 b_1$ | $a_1 b_1$ | $a_0 b_1$ | X | | | |
| PP ₂ : | $a_3 b_2$ | $a_2 b_2$ | $a_1 b_2$ | $a_0 b_2$ | X | X | | |
| PP ₃ : | $a_3 b_3$ | $a_2 b_3$ | $a_1 b_3$ | $a_0 b_3$ | X | X | X | |
| | R ₇ | R ₆ | R ₅ | R ₄ | R ₃ | R ₂ | R ₁ | R ₀ |

$$\text{Let } a_3 a_2 a_1 a_0 \times b_0 = PP_0$$

$$a_3 a_2 a_1 a_0 \times b_1 = PP_1$$

$$a_3 a_2 a_1 a_0 \times b_2 = PP_2$$

$$a_3 a_2 a_1 a_0 \times b_3 = PP_3$$

Summing up the partial products $PP_i, i=0,1,2,3$ with proper weights, the final product is obtained as

$$FP = 8PP_3 + 4PP_2 + 2PP_1 + PP_0$$

Required components



- IC 7495 (4-bit shift register)
- IC 7483 (4-bit adder) - two are required
- IC 74273 (octal +ve edge triggered DFF with active low Master Reset)
- IC 7408 (four 2-input AND gates)
- logic switches to feed in 4-bit multiplicand and multiplier
- logic displays (simple lamps) to read product register

Major steps: i) Load 4-bit multiplier ($b_3 b_2 b_1 b_0$) into shift register IC 7495 and multiplier card ($a_3 a_2 a_1 a_0$) by logic switches
 ii) feed manual clk pulses to IC 7495 and IC 74273

clear product register (74273) to all zeroes.
 clock for 7495 while it is \downarrow for 74273. Invert the clk (fed to 7495) by one or three inverters & feed to 74273.
 After 1st clk pulse: $X: 16PP_0; Y: 0; Z: 8PP_0 (16PP_0/2)$
 2nd clk pulse: $X: 16PP_1; Y: 8PP_0; Z: \frac{1}{2}(16PP_1 + 8PP_0) = 8PP_1 + 4PP_0$
 3rd clk pulse: $X: 16PP_2; Y: 8PP_1 + 4PP_0; Z: \frac{1}{2}(16PP_2 + 8PP_1 + 4PP_0) = 8PP_2 + 4PP_1 + 2PP_0$
 4th clk pulse: $X: 16PP_3; Y: 8PP_2 + 4PP_1 + 2PP_0; Z: \frac{1}{2}(16PP_3 + 8PP_2 + 4PP_1 + 2PP_0) = 8PP_3 + 4PP_2 + 2PP_1 + PP_0 = FP$

Shift register
 (loaded in parallel first, then shift right at each clock pulse)


Four AND gates

  

ignore S₀

$$N.B. Z = \frac{1}{2}(X + Y)$$

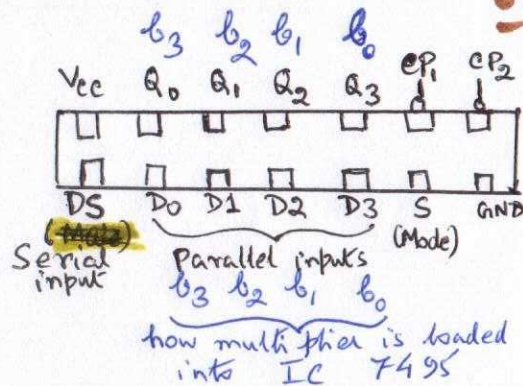i) IC 7495 4-bit shift register with serial and parallel synchronous operating modes




S: mode control input
 $D_0 - D_3$: parallel data inputs
 DS: serial data input
 \overline{CP}_1 : serial clock (active low going edge) input
 \overline{CP}_2 : parallel clock (active low going edge) input
 $Q_0 - Q_3$: parallel outputs

• When S is HIGH ("1"), \overline{CP}_2 is enabled. A hi-to-lo (\downarrow) transition on enabled \overline{CP}_2 transfers parallel data from the $P_0 - P_3$ inputs to the $Q_0 - Q_3$ outputs (parallel load).
 • When S is LOW ("0"), \overline{CP}_1 is enabled. A high-to-low (\downarrow) transition on enabled \overline{CP}_1 transfers the data from serial input (DS) to Q_0 , and shifts the data from Q_0 to Q_1 , Q_1 to Q_2 , and Q_2 to Q_3 respectively (right shift).

• For normal operation, S should be allowed to change states when both the clock i/p's are low.
 N.B. Keep \overline{CP}_1 and \overline{CP}_2 stroked as parallel load & right shift are to occur at different times.

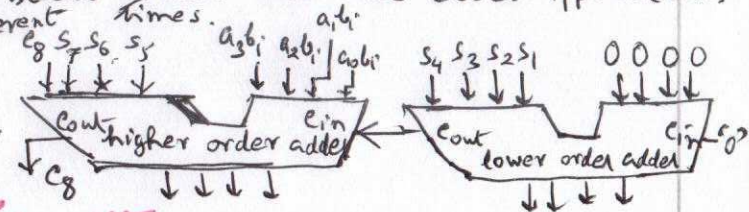ii) IC 7483 - 4-bit parallel adder with Cin, Cout

The two adders will be connected in cascade as shown here \Rightarrow



ii) IC 74273 - octal positive edge triggered DFFs with active low clear (\overline{MR}) input:

note that the FFs in 74273 are positive edge triggered whereas the FFs in 7495 are negative edge triggered. So, one can generate clk for 7495 by way of logic switch, and invert this signal using one or better three inverters (to provide adequate delay) and feed the inverted clock to \overline{CP} input of 74273.

iii) IC 7408 - quad 2-input NAND gates

iv) use logic display (simple lamps) to read the value of the contents of the product register IC 74273