

EC 39003 (Digital Electronic Circuits Lab)	End-Semester Laboratory Test, 2020
Dept. of Electronics and Electrical Comm. Engineering	IIT Kharagpur
Wednesday batch Full Marks: 30	Time: 1 Hour Date: 18.11.2020

Submit Test answer script and Circuit file on Moodle. Name both files as

“**ROLL_Number_BD1.pdf**” and “**ROLL_Number_BD1.CKT**”.

* Please stick to deadline. **Unnecessary delay in submission time stamp of circuit file will attract penalty.**

Report should consist of the following items.

1. Name (in CAPITAL)
2. Roll Number
3. Problem statement (**BD1=** , **BD2=[0:MC]**, **MC=**)
4. Circuit Diagram
5. Discussion

OBJECTIVE:

Implement and **simulate** (in **Circuit Maker** software) a **BCD (binary-coded decimal) adder** that adds two single-digit BCD numbers **BD1** and **BD2** with proper **correction**.

Let “**p**” be the least significant decimal digit of your Roll number. Then

$$\begin{aligned}
 \mathbf{BD1} &= \mathbf{9 - p} \quad (\text{if } 0 \leq p \leq 2) \\
 &= \mathbf{p + 4} \quad (\text{if } 3 \leq p \leq 5) \\
 &= \mathbf{p} \quad (\text{otherwise})
 \end{aligned}$$

Whereas, **BD2** will be the output of an **up-counter** which counts from 0 up to the maximum count **MC**, such that

$$\begin{aligned}
 \mathbf{MC} &= \mathbf{BD1 + 5} \quad (\text{if } \mathbf{BD1} \leq 4) \\
 &= \mathbf{BD1} \quad (\text{otherwise})
 \end{aligned}$$

You are allowed to use only **IC 7493** as the up-counter.

Display the result at (slow clock speed) at each step on **7-segment (common anode) LED**.